

Group 28

Kandula Revanth (21CS10035)

Pola Gnana Shekar (21CS10052)

Control signals used:

- ❖ readIn: controls reading of next instruction
 - 1 - read next instruction
 - 0 - don't read
- ❖ MuxAlu1: select between regA and PC instruction
 - 1 - select regA
 - 0 - select PC
- ❖ MuxAlu2: select between regB and immediate value
 - 1 - select regB
 - 0 - select imm
- ❖ writeDM: write to Data Memory
 - 1 - write to Data Memory
 - 0 - don't write
- ❖ readDM: read from Data Memory
 - 1 - read from Data Memory
 - 0 - don't read
- ❖ muxWB: select between AluOut and value from LMD
 - 1 - select AluOut
 - 0 - select value from LMD
- ❖ writeReg: controls write action in register bank
 - 1 - write to register
 - 0 - don't write
- ❖ rst: resets all the values
 - 1 - reset all
 - 0 - no need to reset
- ❖ branch: used to select type of branching (BR / BMI / BPL / BZ)
 - 000 - No branching

001 - BR

010 - BMI

011 - BPL

100 - BZ

❖ aluFunc: used to select the arithmetic operation that to be performed.

0000 - ADD

0001 - SUB

0010 - NOT

0011 - AND

0100 - OR

0101 - XOR

0110 - SLL

0111 - SRL

1000 - SRA

Control Signal Table:

	readIn	MuxAl u1	MuxAl u2	writeD M	readD M	muxW B	writeRe g	rst	branch	aluFun c
ADD	1	1	1	0	0	1	1	0	000	0000
SUB	1	1	1	0	0	1	1	0	000	0001
NOT	1	1	1	0	0	1	1	0	000	0010
AND	1	1	1	0	0	1	1	0	000	0011
OR	1	1	1	0	0	1	1	0	000	0100
XOR	1	1	1	0	0	1	1	0	000	0101
SLL	1	1	1	0	0	1	1	0	000	0110
SRL	1	1	1	0	0	1	1	0	000	0111
SRA	1	1	1	0	0	1	1	0	000	1000
ADDI	1	1	0	0	0	1	1	0	000	0000
SUBI	1	1	0	0	0	1	1	0	000	0001

NOTI	1	1	0	0	0	1	1	0	000	0010
ANDI	1	1	0	0	0	1	1	0	000	0011
ORI	1	1	0	0	0	1	1	0	000	0100
XORI	1	1	0	0	0	1	1	0	000	0101
SLLI	1	1	0	0	0	1	1	0	000	0110
SRLI	1	1	0	0	0	1	1	0	000	0111
LD	1	1	0	0	1	0	1	0	000	0000
ST	1	1	0	1	0	0	0	0	000	0000
LDSP	1	1	0	0	1	0	1	0	000	0000
STSP	1	1	0	1	0	0	0	0	000	0000
BR	1	0	0	0	0	0	0	0	001	0000
BMi	1	0	0	0	0	0	0	0	010	0000
BPL	1	0	0	0	0	0	0	0	011	0000
BZ	1	0	0	0	0	0	0	0	100	0000
PUSH	1	1	0	1	0	0	1	0	000	0001
POP	1	1	0	0	1	0	1	0	000	0000
CALL	1	1	0	1	0	0	1	0	000	0001
RET	1	1	0	0	1	0	1	0	000	0000
MOVE	1	1	0	0	0	1	1	0	000	0000
NOP	1	0	0	0	0	0	0	0	000	0000
HALT	0	0	0	0	0	0	0	1	000	0000

RTL instruction Table:

Instruction	RTL micro operations	Control Signals
ADD	- Source and Destination registers obtained from 32 bit Instruction.	- - MuxAlu1,MuxAlu2

	<ul style="list-style-type: none"> - Select the reg1 and reg2 as operands - Perform addition using aluFunc signal. - Select AluOut to write back. - Write back in register bank 	<ul style="list-style-type: none"> - aluFunc - muxWB - writeReg
ADDI	<ul style="list-style-type: none"> - Source and Destination registers and immediate value obtained from 32 bit Instruction. - Select the reg1 and imm as operands - Perform addition using aluFunc signal. - Select AluOut to write back. - Write back in register bank 	<ul style="list-style-type: none"> - MuxAlu1,MuxAlu2 - aluFunc - muxWB - writeReg
LD	<ul style="list-style-type: none"> - Obtain source and Destination register from 32-bit instruction. - Read from data memory - Load from LMD for write back - Perform write back in register bank. 	<ul style="list-style-type: none"> - readDM - muxWB - writeReg
ST	<ul style="list-style-type: none"> - Obtain source and destination register from 32-bit instruction. - write to data memory 	<ul style="list-style-type: none"> - writeDM
BMI	<ul style="list-style-type: none"> - Source register and offset are obtained from instruction. - Branch if less than zero is selected using branch - Update PC according to the condition. 	<ul style="list-style-type: none"> - branch
MOVE	<ul style="list-style-type: none"> - Dest and src registers are obtained from instruction. - Perform add operation with one operand as src register and zero register. - Select aluOut for write back. - Perform write back. 	<ul style="list-style-type: none"> - MuxAlu1,MuxAlu2 - aluFunc - muxWB - writeReg
CALL	<ul style="list-style-type: none"> - Immediate value from instruction. - Perform add operation to the PC and 4. - Store it in stack mem - Perform addition of PC and offset - Update this as next PC. 	<ul style="list-style-type: none"> - writeDm
RET	<ul style="list-style-type: none"> - Perform read from stack mem. - Update this to PC. 	<ul style="list-style-type: none"> - readDM

Data Path:

